

DEEPTHI SUDHARSAN (CB.EN.U4AIE19022)

S ISHA INDHU (CB.EN.U4AIE19030)

LAKSHAYA KARTHIKEYAN (CB.EN.U4AIE19039)

INVERTING AND NON INVERTING OPERATIONAL AMPLIFIERS



CSE-AI , AMRITA VISHWA VIDYAPEETHAM , COIMBATORE

AMRITA VISHWA VIDYAPEETHAM , AMRITANNAGAR P.O. , COIMBATORE – 641 112

Table of Contents

Aim.....	[03]
Theory.....	[03]
Operational Amplifiers.....	[03]
Inverting Op-Amps.....	[04]
Non-inverting Op-Amps.....	[04]
Challenge 1.....	[06]
Challenge 2.....	[17]
Inference.....	[27]
Conclusion.....	[13]
References.....	[29]
Acknowledgment.....	[29]

Aim:

The aim of this project is to implement both inverting and noninverting operational amplifier (op amp) circuits using ADALM1000 and obtain accurate results.


Theory:Operational Amplifiers:

An operational amplifier multiplies the voltage difference between its non-inverting and inverting inputs with a gain A and outputs this value. The equation representing this is:

$$V_{out} = A(V_{in}^+ - V_{in}^-)$$


Where V_{in}^+ is non-inverting and V_{in}^- is inverting.

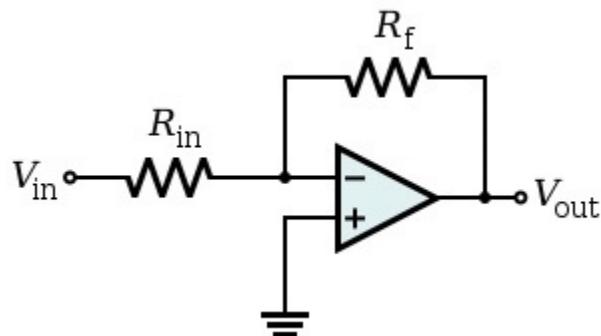OP-AMPS are used with feedback resistors so as to control the gain as shown.




Inverting OP-AMP:

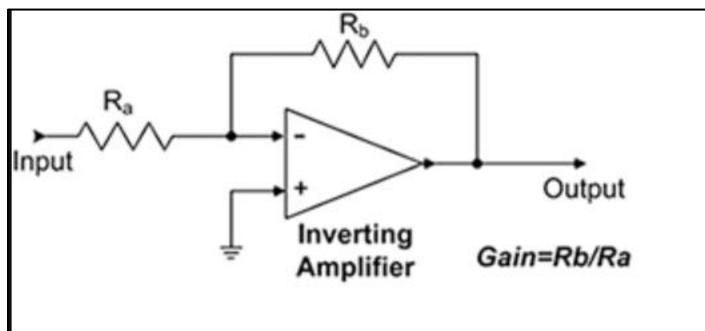The output of this circuit is out of phase with its input by 180° . Consequently the output is an inverted and amplified version of the input. Two external resistors are used to create a feedback circuit and make a closed loop circuit across the amplifier.



Gain of inverting op-amp will be:

$$\text{Gain} = \frac{V_{out}}{V_{in}} = -\frac{R_f}{R_{in}}$$

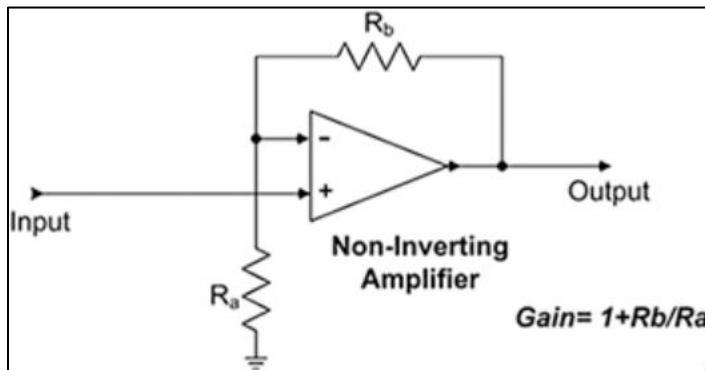Non-Inverting Op-Amp:

The output signal is in-phase with the input signal.


$$\frac{V_{in}}{V_{out}} = \frac{R1}{(R1 + R_f)}$$

$$A = \frac{V_{out}}{V_{in}} = \frac{R1 + R_f}{R1}$$


Materials required:

- ADALM1000 hardware module
- Solder-less breadboard and jumper wire kit
- AD8542 devices (CMOS rail-to-rail amplifier)
- $1\text{k}\Omega$ and 470Ω resistors

Pin Diagram AD542:

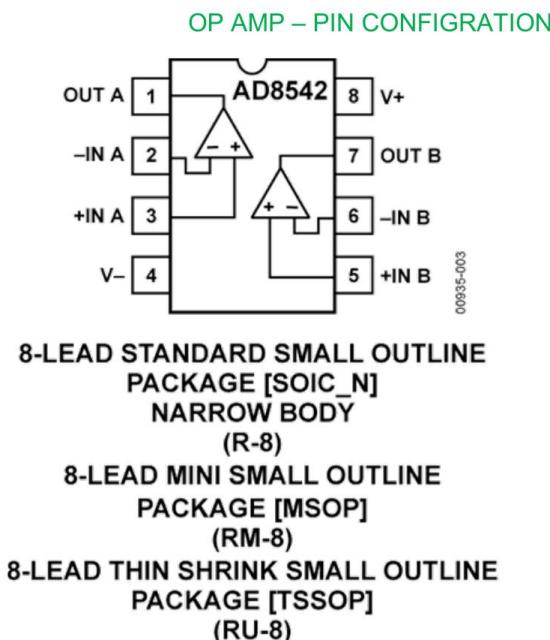

Challenge 1: Non-inverting

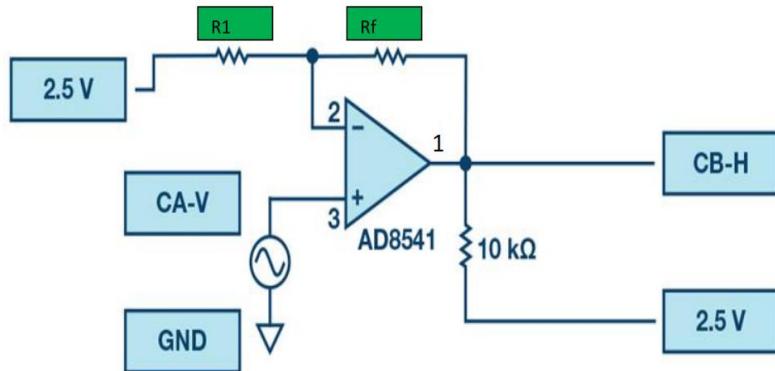


Procedure:

1. Connect the circuit according to the diagram above.
2. In order to get the gain in a non-inverting amplifier, we use $A=1+R_f/R_{in}$.
3. Taking different values of R_{in} , use the above formula to calculate gain(A).
4. Record the values in a table, shown as the P-P value in CA and CB.
5. Check if the ratio of obtained channel B voltage to channel A voltage is equal to the calculated gain
6. Check if channel B is equal to calculated gain*Vin

R _f	R _{in}	Calculated gain = $1 + \frac{R_f}{R_1}$	Channel A	Channel B	Voltage gain= (ChB/ChA)	V _{out} =A*V _{in} where A=gain
1000	470	3.12	1.00	3.113	3.113	$3.113=3.12*1$
1000	1000	2	1.0006	2.0045	2	$2.0045=2*1.0006$
1000	20000	1.05	1.00	1.0504	1.05	$1.0504=1.05*1.00$


Screenshots:

Setting for all three shapes & cases:

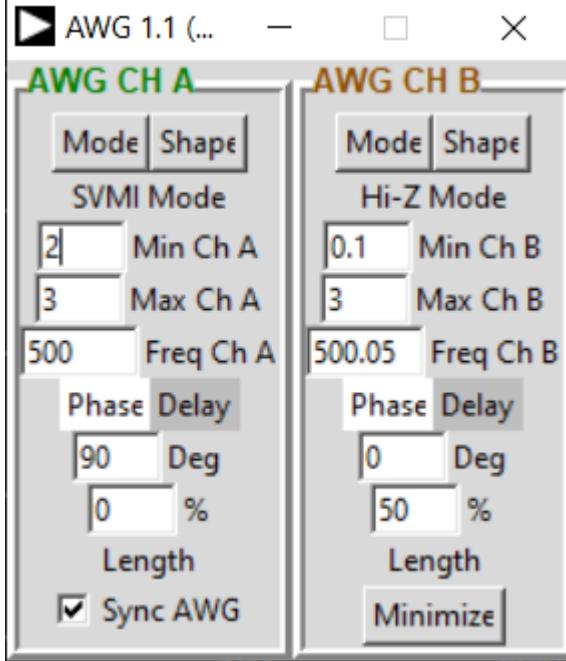

Case 1:

SINE

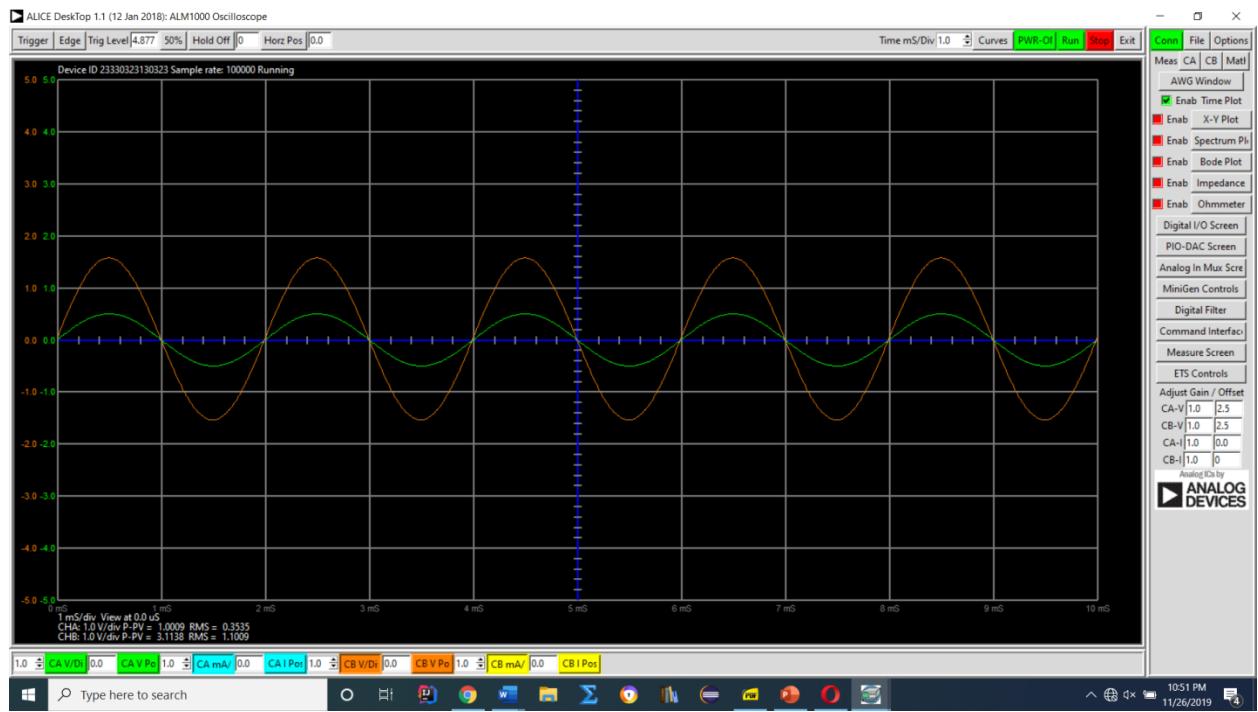


Calculation:

$$R_1 = 470$$

$$R_f = 1000$$

$$\text{Gain} = 1 + 1000/470 = 3.12$$

$$\text{Obtained voltage gain} = \text{CH B}/\text{CH A} = 3.113/1.00 = 3.113$$

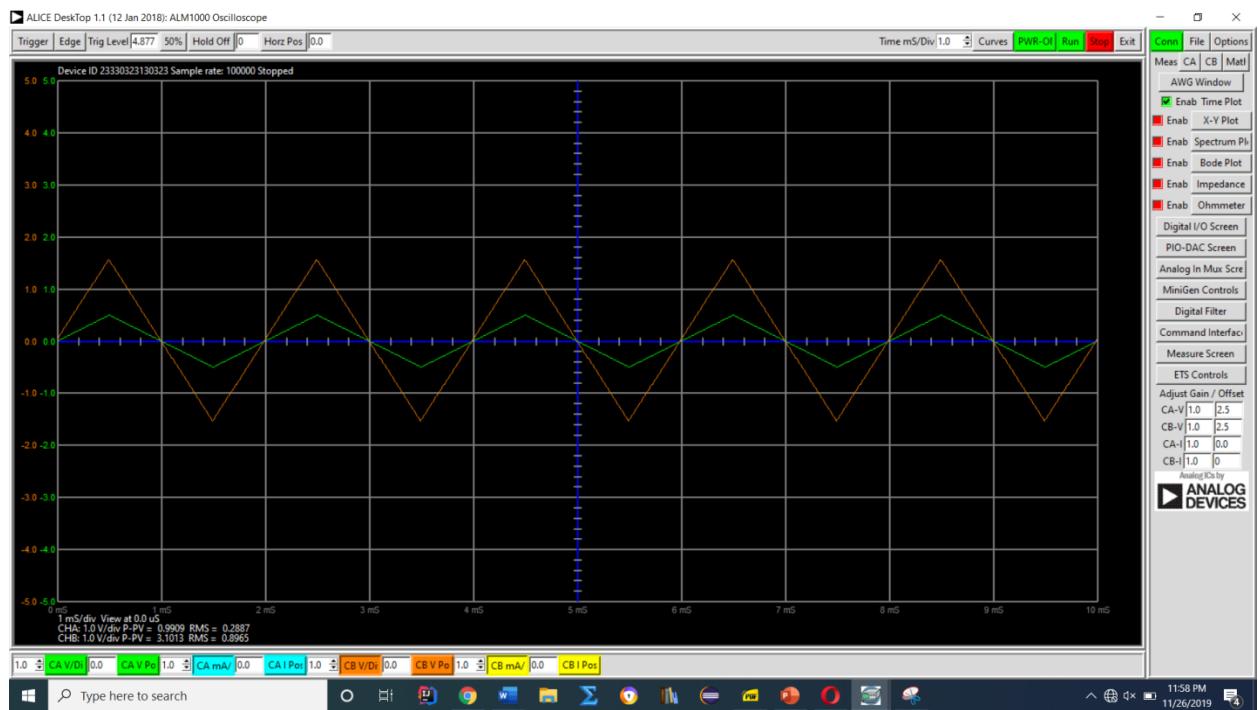TRIANGLE


Calculations:

$$R_1 = 470$$

$$R_f = 1000$$

$$\text{Gain} = 1 + 1000/470 = 3.12$$

$$\text{Obtained voltage gain} = \text{CH B}/\text{CH A} = 3.1013/0.9909 = 3.129$$

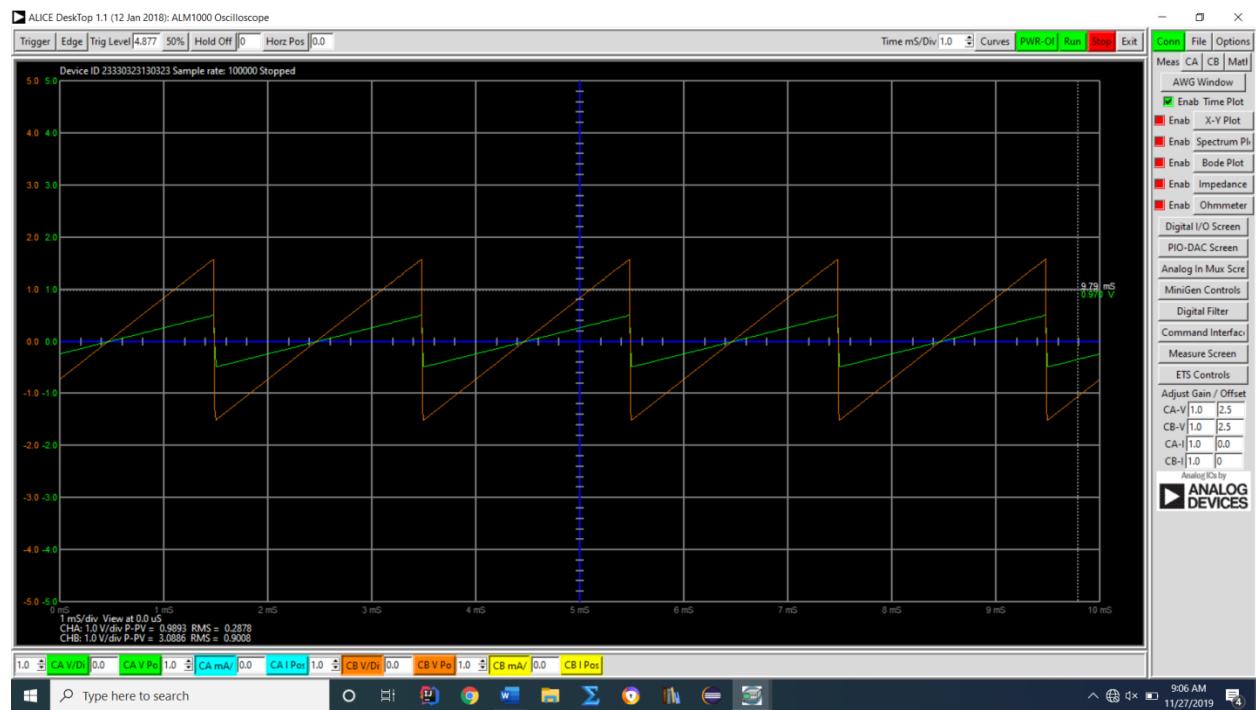SAWTOOTH

Calculations:

$$R_1 = 470$$


$$R_f = 1000$$

$$\text{Gain} = 1 + 1000/470 = 3.12$$

$$\text{Obtained voltage gain} = \text{CH B}/\text{CH A} = 3.0886/0.9893 = 3.122$$

Case 2:

SINE

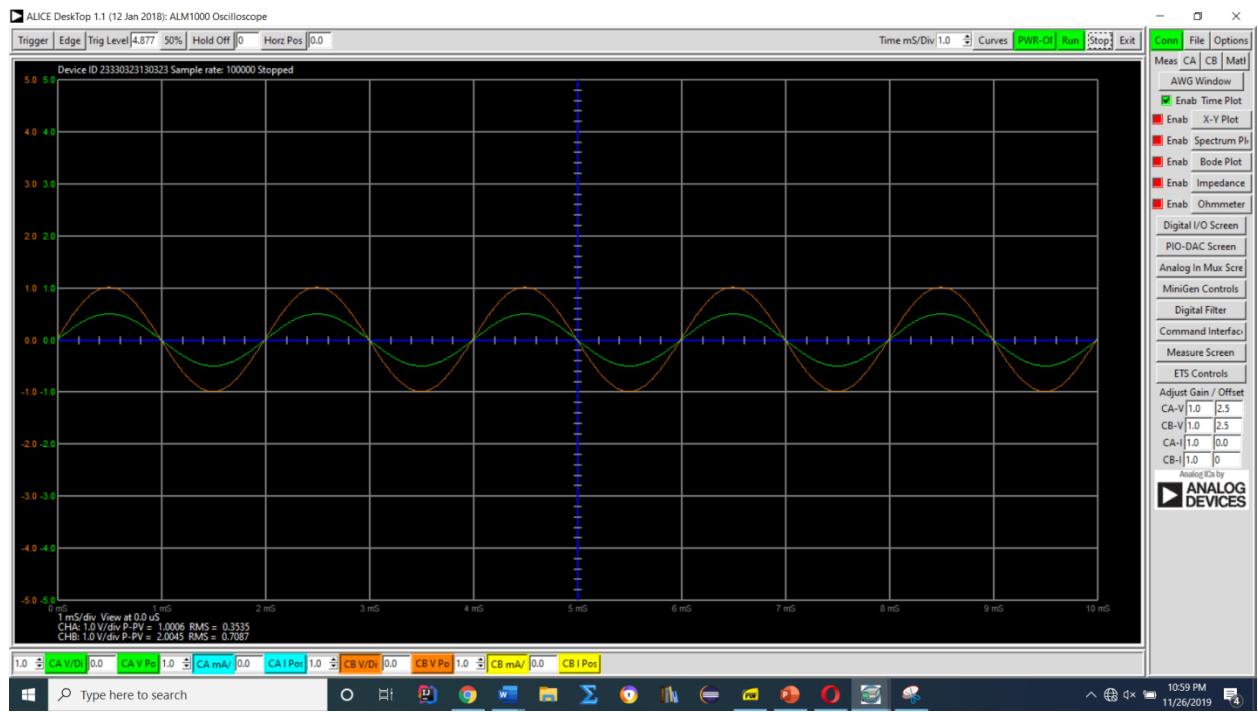

Calculations:


$$R_1 = 1000$$

$$R_f = 1000$$

$$\text{Gain} = 1 + 1000/1000 = 1+1=2$$

$$\text{Obtained gain} = \text{CHB/CHA} = 2.0045/1.0006 = 2$$

SAWTOOTH

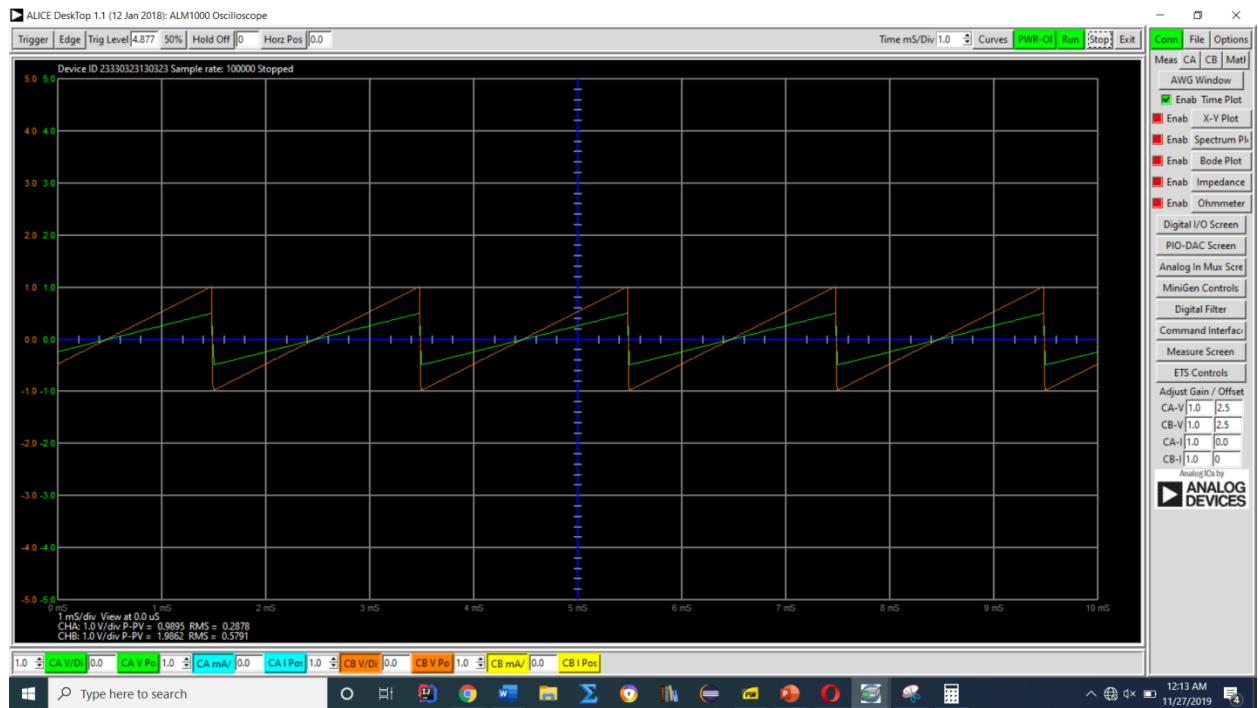

Calculations:


$$R_1 = 1000$$

$$R_f = 1000$$

$$\text{Gain} = 1 + 1000/1000 = 1 + 1 = 2$$

$$\text{Obtained gain} = \text{CHB}/\text{CHA} = 1.9862/0.9895 = 2.007$$

TRIANGLE

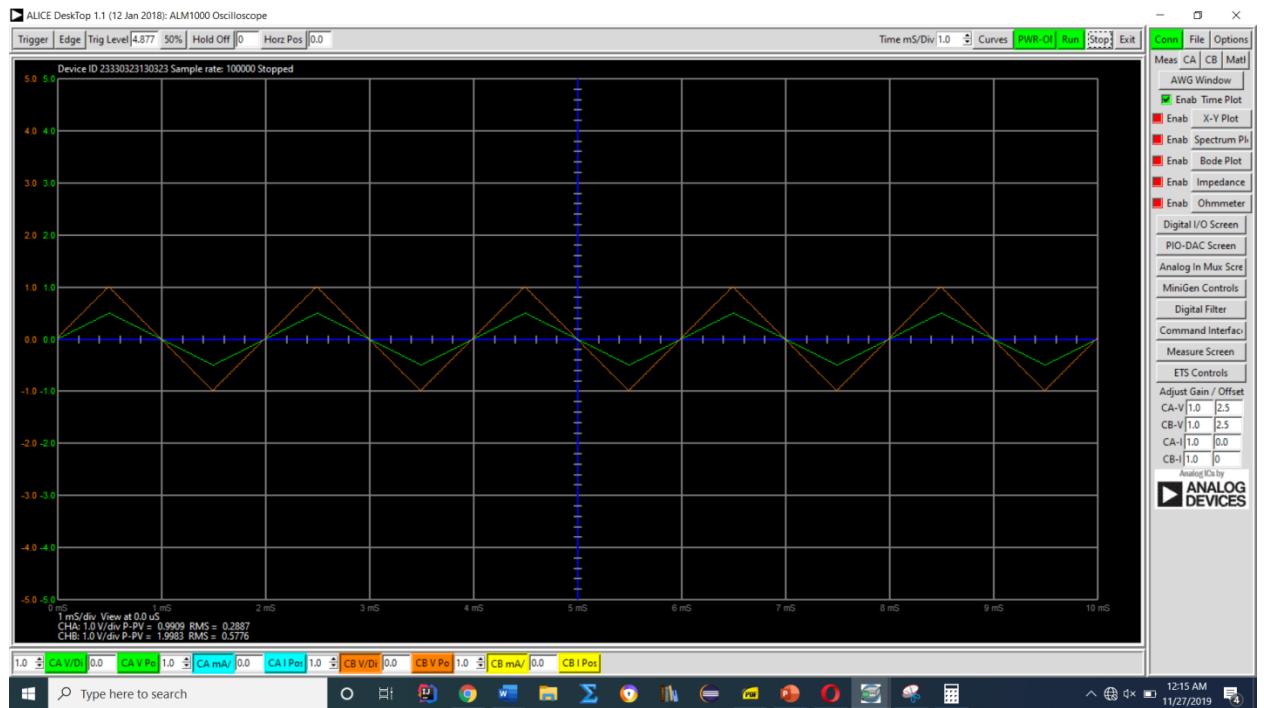

Calculations:

R1=1000


Rf=1000

$$\text{Gain} = 1 + 1000/1000 = 1 + 1 = 2$$

Obtained gain=CHB/CHA =1.9983/0.9909=2.01

Case 3:

SINE

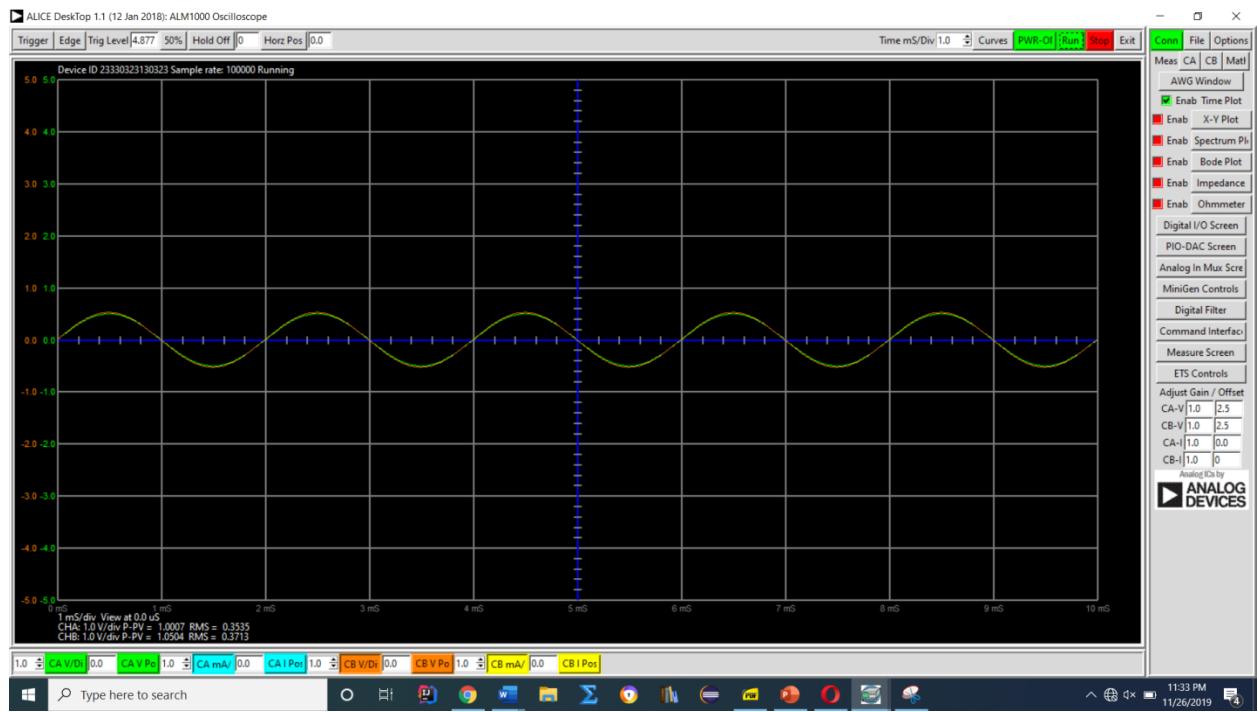

Calculations:


$$R_1 = 20000$$

$$R_f = 1000$$

$$\text{Gain} = 1 + R_f/R_1 = 1 + 1000/20000 = 1.05$$

$$\text{Obtained Gain} = CHB/CHA = 1.0504$$

SAWTOOTH

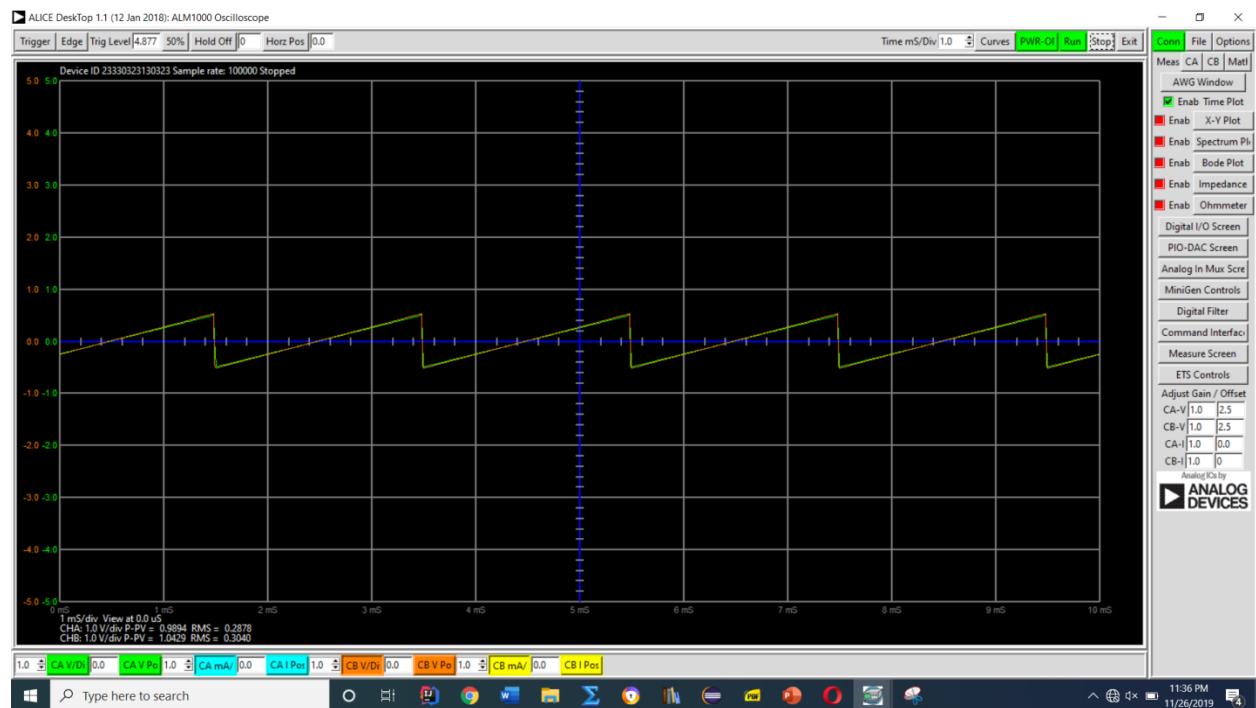

Calculations:


$$R_1 = 20000$$

$$R_f = 1000$$

$$\text{Gain} = 1 + R_f/R_1 = 1 + 1000/20000 = 1.05$$

$$\text{Obtained Gain} = \text{CHB}/\text{CHA} = 1.0429/0.9894 = 1.05$$

TRIANGLE

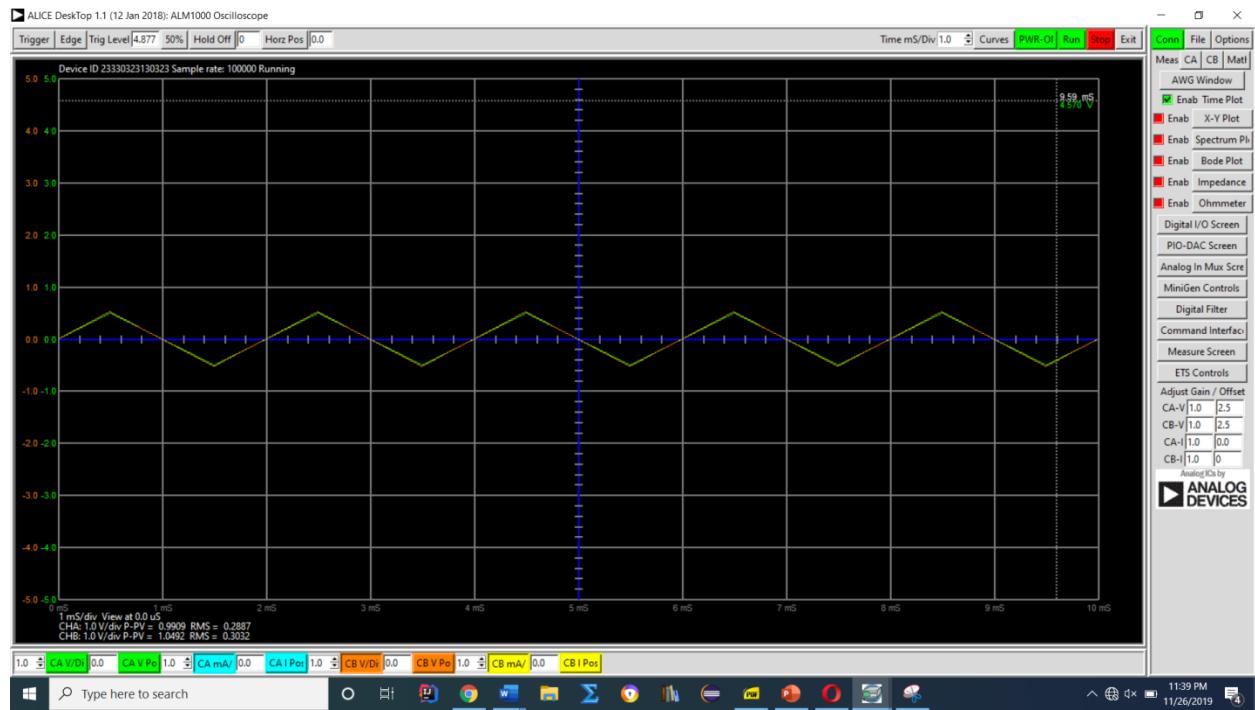

Calculations:



R1=20000

Rf=1000

$$\text{Gain} = 1 + R_f/R_1 = 1 + 1000/20000 = 1.05$$

Obtained Gain = CHB/CHA = 1.042/0.9909 = 1.05

Challenge 2 : Inverting

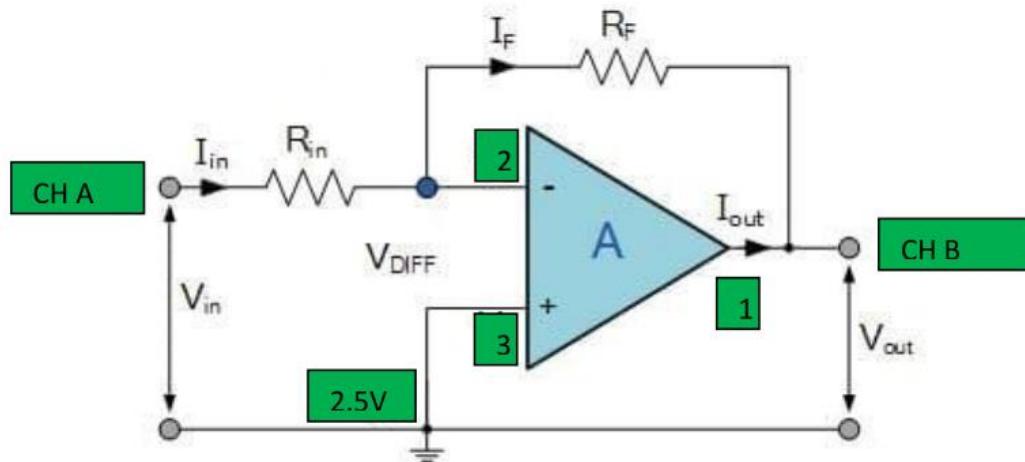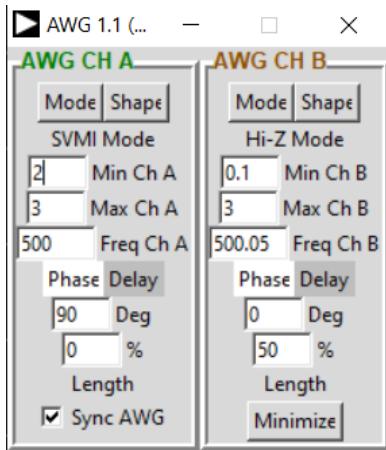


Procedure:

1. Connect the circuit according to the diagram above.
2. In order to get the gain in a inverting amplifier, we use $A = R_f/R_{in}$.
3. Taking different values of R_{in} , use the above formula to calculate gain(A).
4. Record the values in a table, shown as the P-P value in CA and CB.
5. Check if the ratio of obtained channel B voltage to channel A voltage is equal to the calculated gain
6. Check if channel B is equal to calculated gain * V_{in}

Rf	Rin	Calculated gain = $1 + \frac{R_f}{R_1}$	Channel A	Channel B	Voltage gain= (ChB/ChA)	Vout=A*Vin Where A is gain
1000	470	2.12	0.9909	2.1145	2.12	$2.1145 = 2.1146 * 0.9909$
1000	1000	1	1.006	1.002	1	$1.002 = 1 * 1.006$
1000	20000	0.05	1.0008	0.0504	0.05	$0.0504 = 0.05 * 1.0008$

Case 1:

SINE

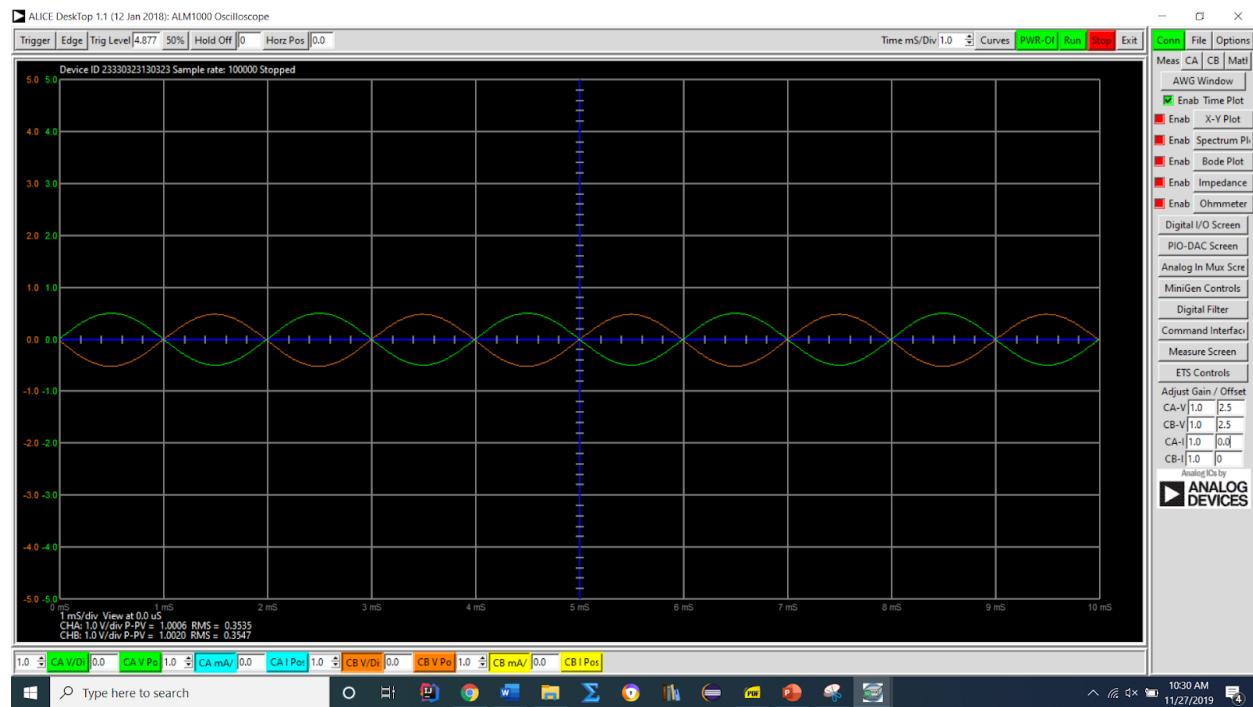


$$R_1 = 1000$$

$$R_f = 1000$$

$$\text{Gain} = -R_f/R_1 = 1$$

$$\text{Obtained Gain} = \text{CHB/CHA} = 1.002/1.006 = 1.00$$

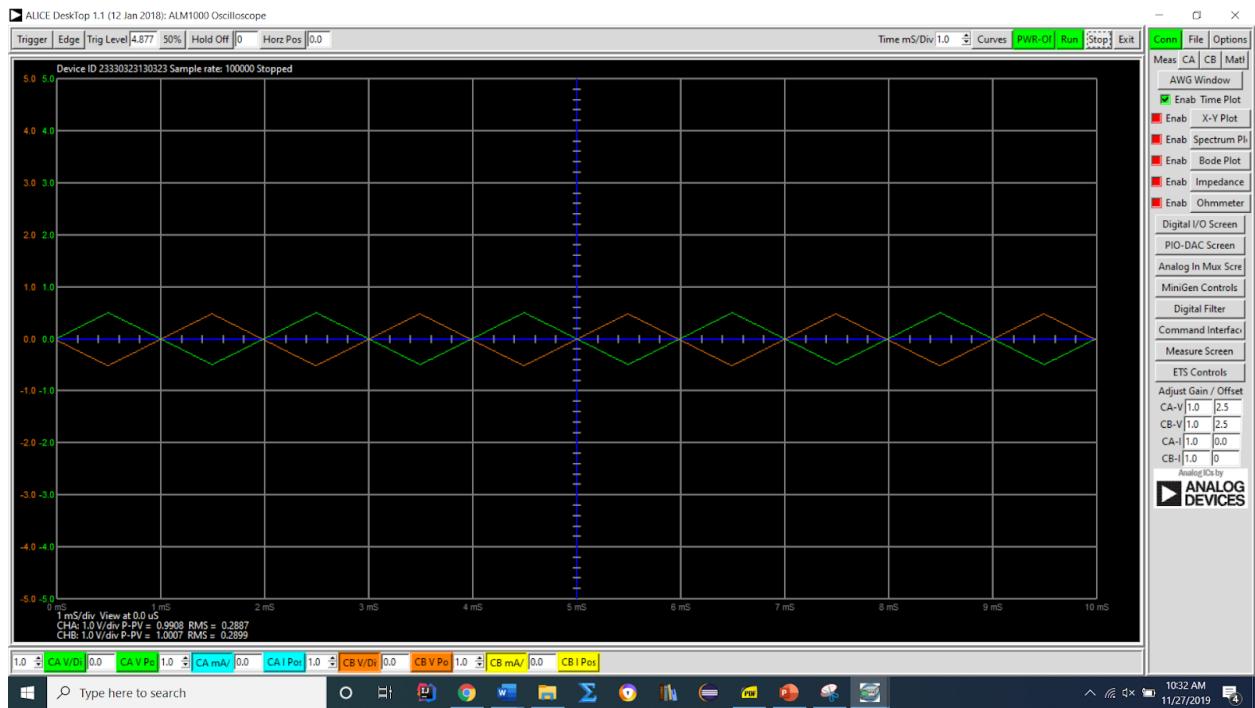TRIANGLE


$$R_1 = 1000$$

$$R_f = 1000$$

$$\text{Gain} = -R_f/R_1 = 1$$

$$\text{Obtained gain} = CHB/CHA = 1.007/0.9908 = 1.01$$

SAWTOOTH

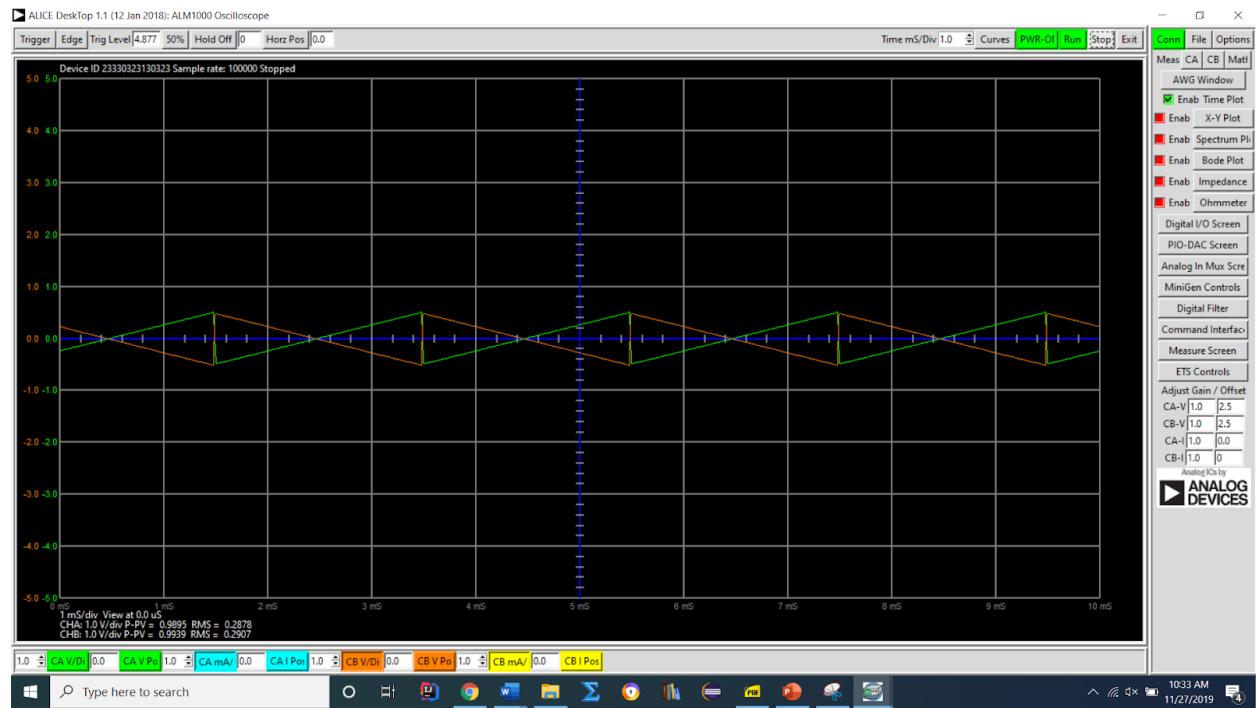


Calculations:

$$R_1 = 1000$$

$$R_f = 1000$$

$$\text{Gain} = -R_f/R_1 = 1$$

$$\text{Obtained gain} = CH_B/CH_A = 0.9939/0.9895 = 1.00$$

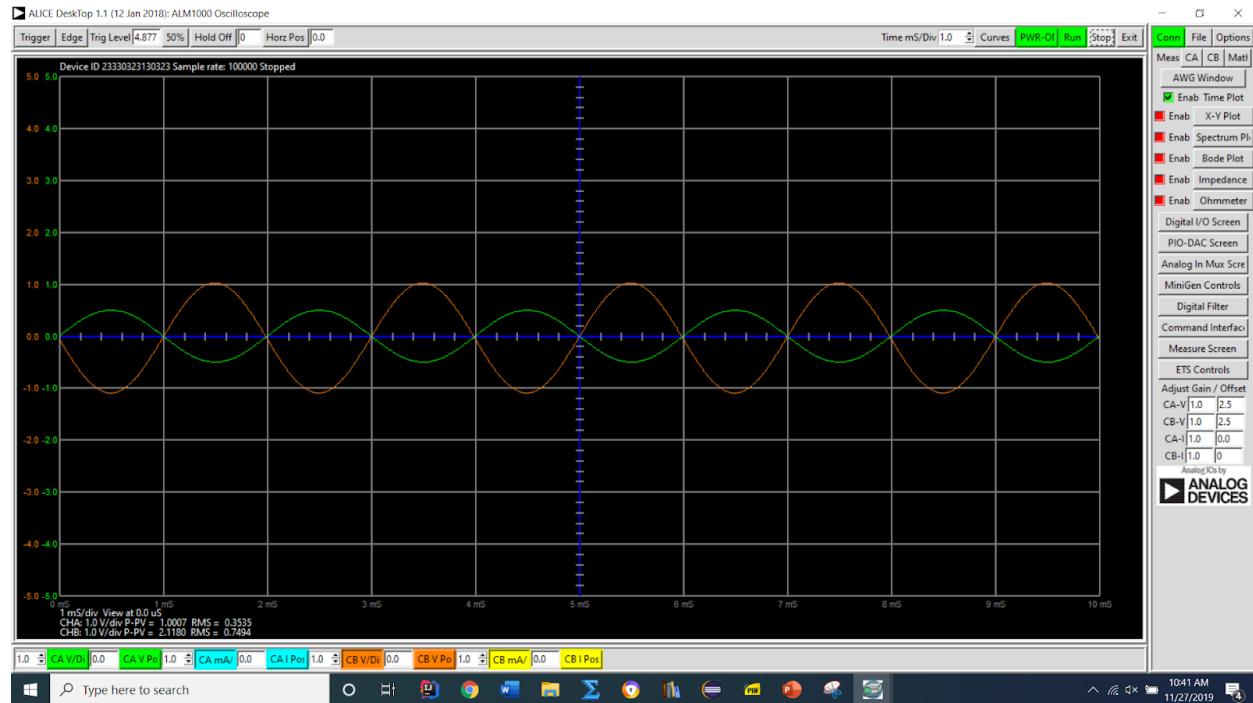CASE 2:*SINE***Calculations:**


$$R_1 = 470$$

$$R_f = 1000$$

$$\text{Gain} = 1000/470 = 2.12$$

$$\text{Obtained Gain} = 2.118/1.00 = 2.12$$

TRIANGLE

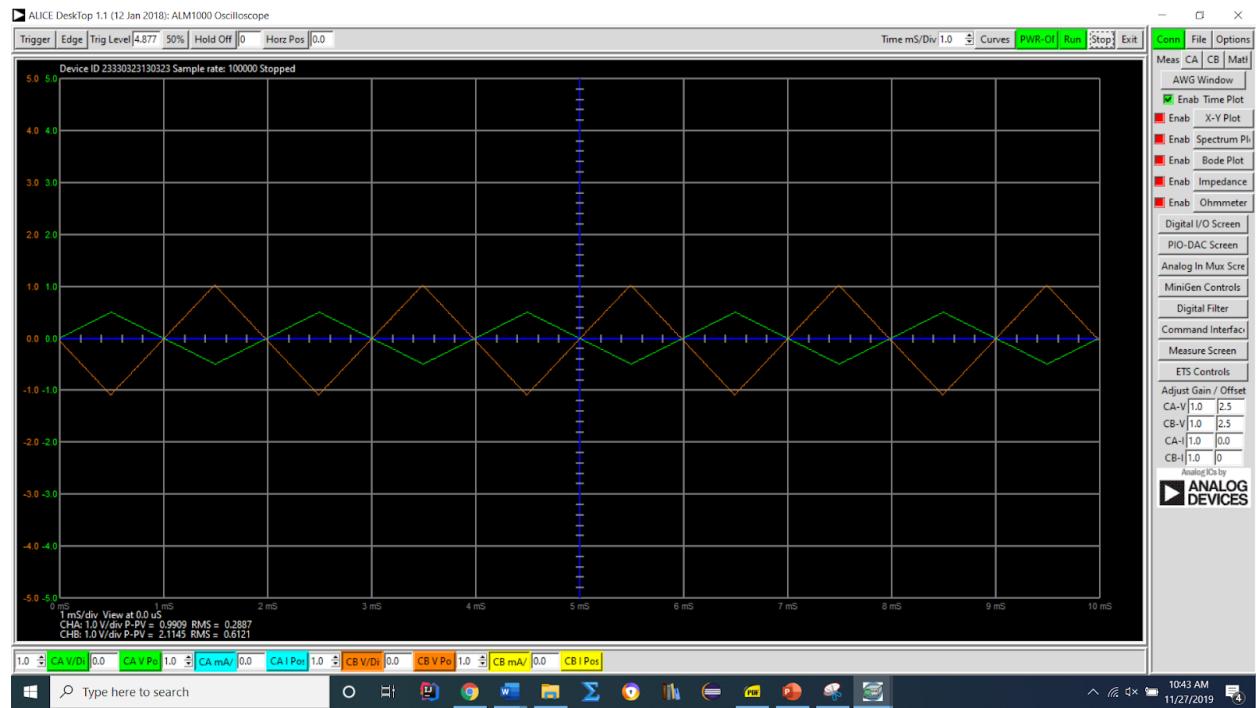

Calculations:


$$R_1 = 470$$

$$R_f = 1000$$

$$\text{Gain} = 1000/470 = 2.12$$

$$\text{Obtained Gain} = 2.1145/0.9909 = 2.13$$

SAWTOOTH

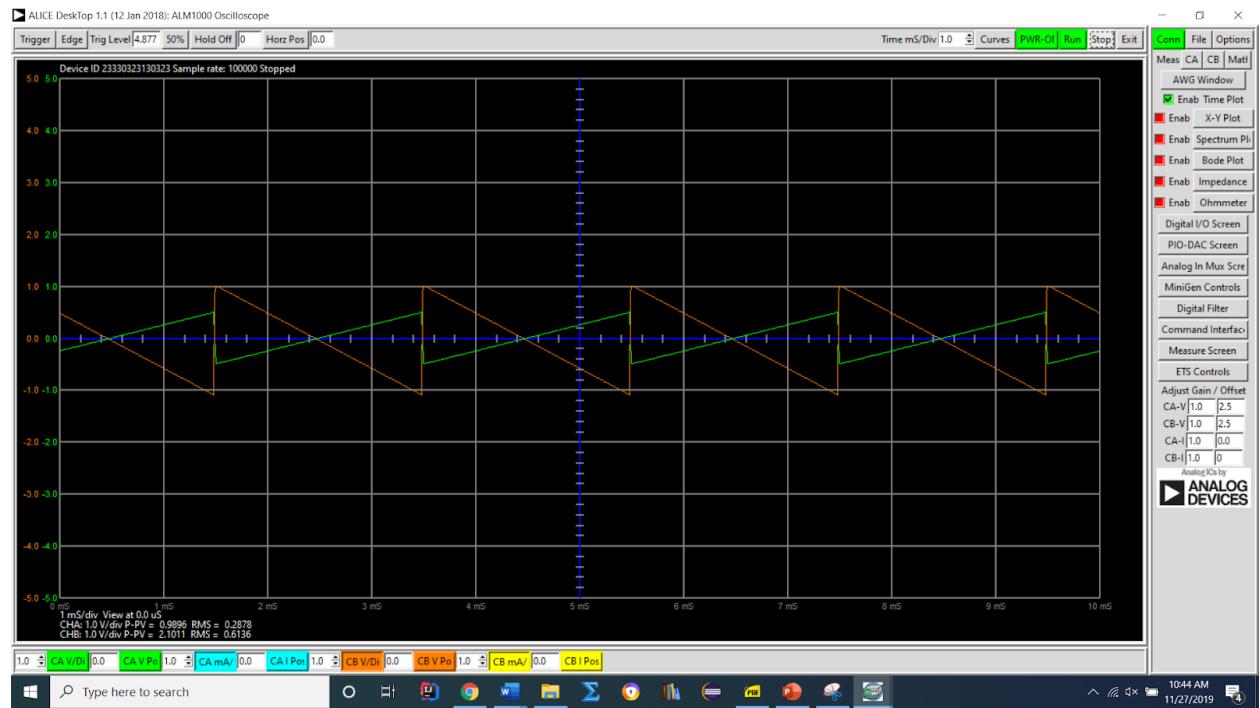


Calculations:

$$R_1 = 470$$

$$R_f = 1000$$

$$\text{Gain} = 1000/470 = 2.12$$

$$\text{Obtained Gain} = 2.1011/0.9896 = 2.12$$

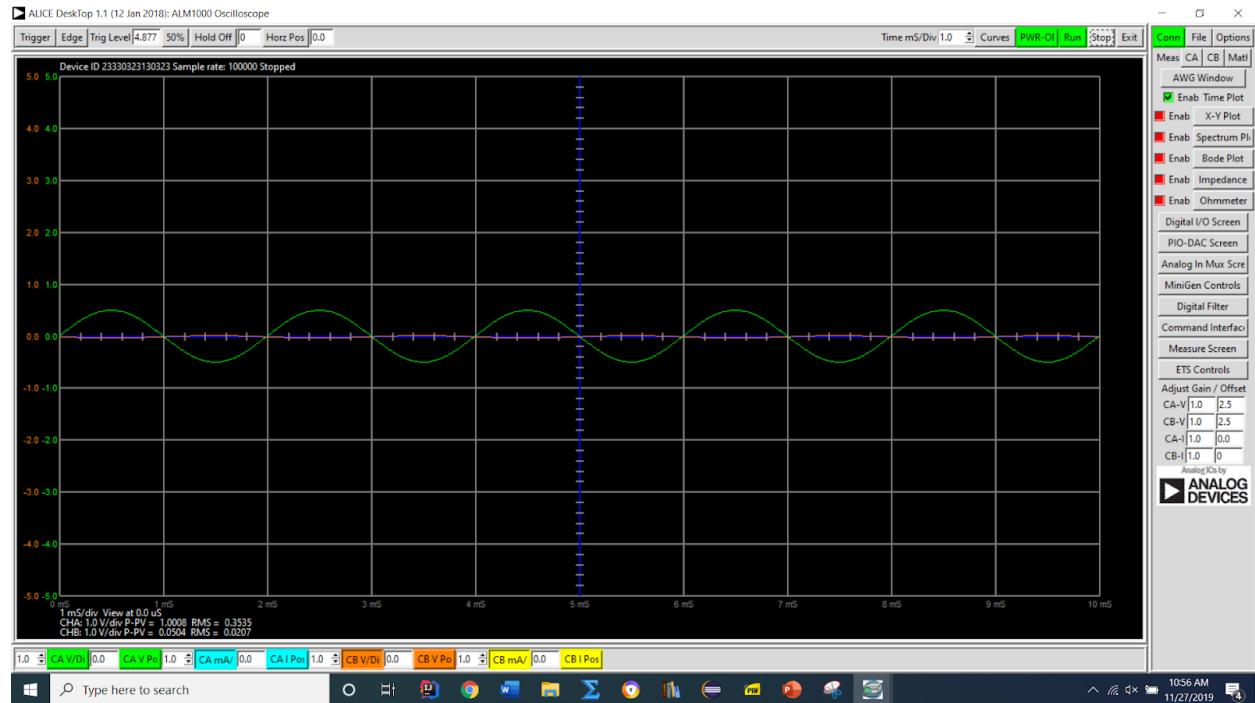CASE 3:*SINE*


$$R_1 = 20000$$

$$R_f = 1000$$

$$\text{Gain} = 1000/20000 = 0.05$$

$$\text{Obtained gain} = 0.0504/1.0008 = 0.05$$

TRIANGLE

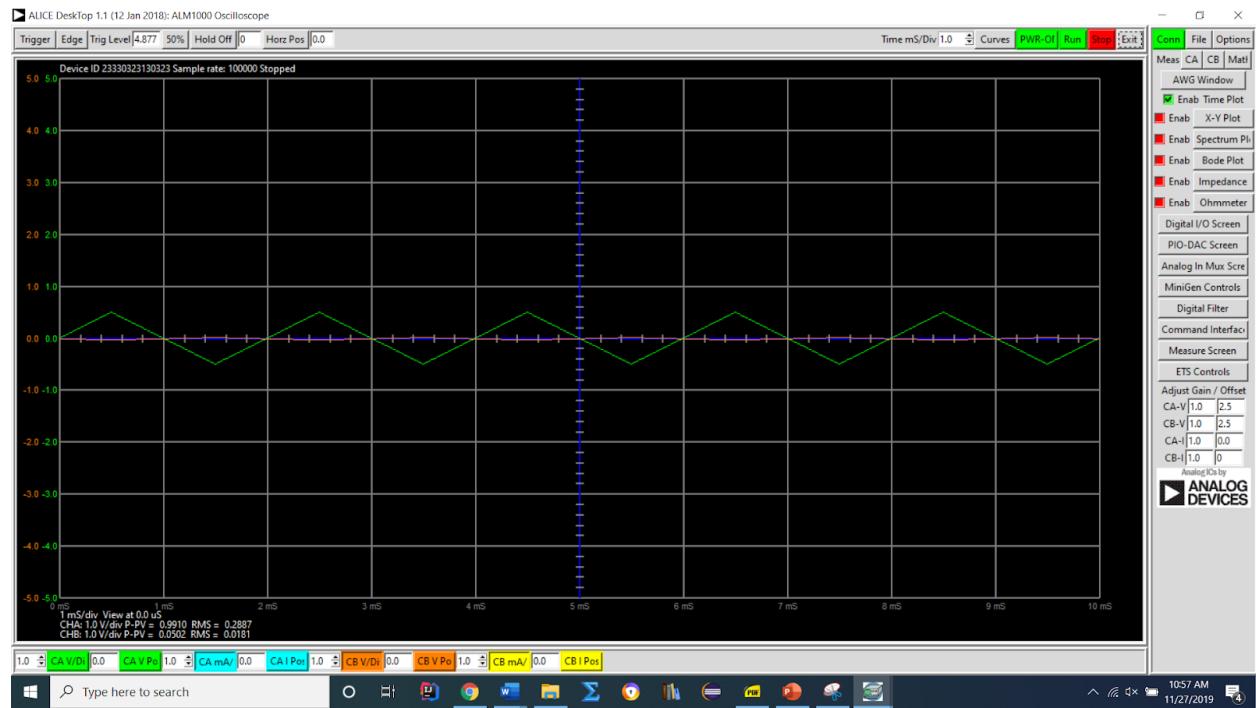

Calculations:


$$R_1 = 20000$$

$$R_F = 1000$$

$$\text{Gain} = 1000/20000 = 0.05$$

$$\text{Obtained Gain} = 0.0502/0.9910 = 0.05$$

SAWTOOTH

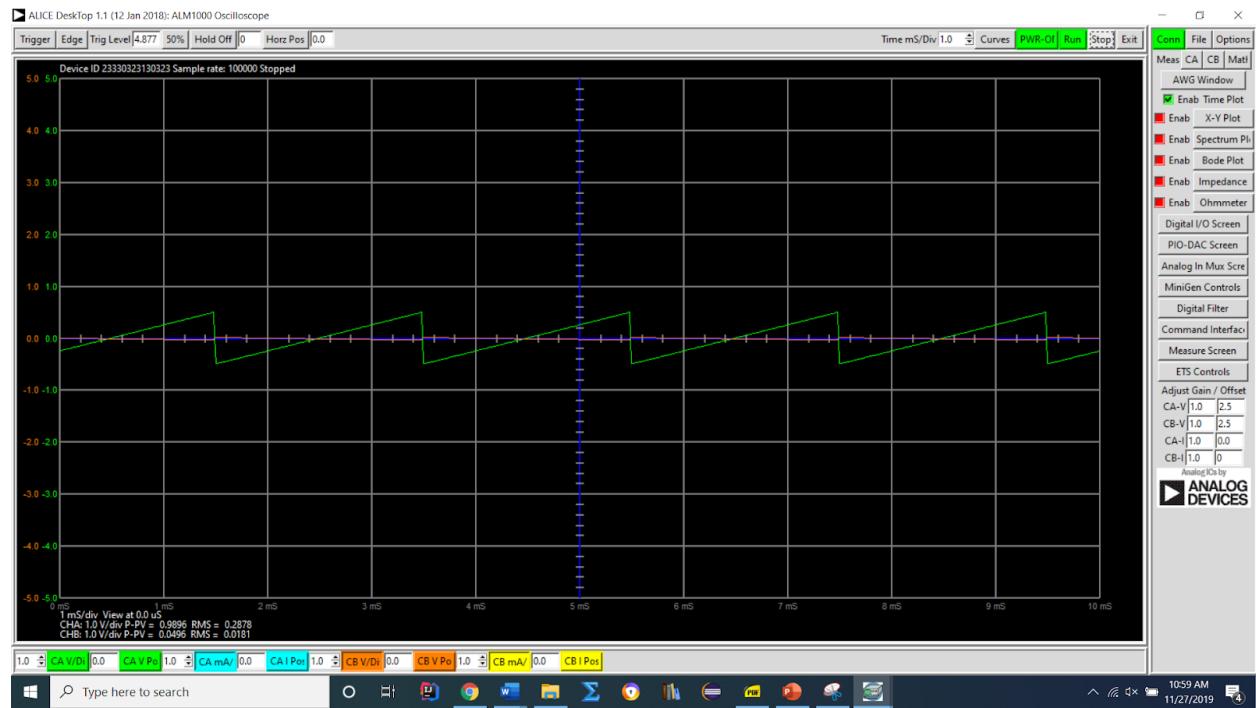

Calculations:


$$R_1 = 20000$$

$$R_F = 1000$$

$$\text{Gain} = 1000/20000 = 0.05$$



$$\text{Obtained Gain} = 0.0496/0.9896 = 0.05$$

Inference

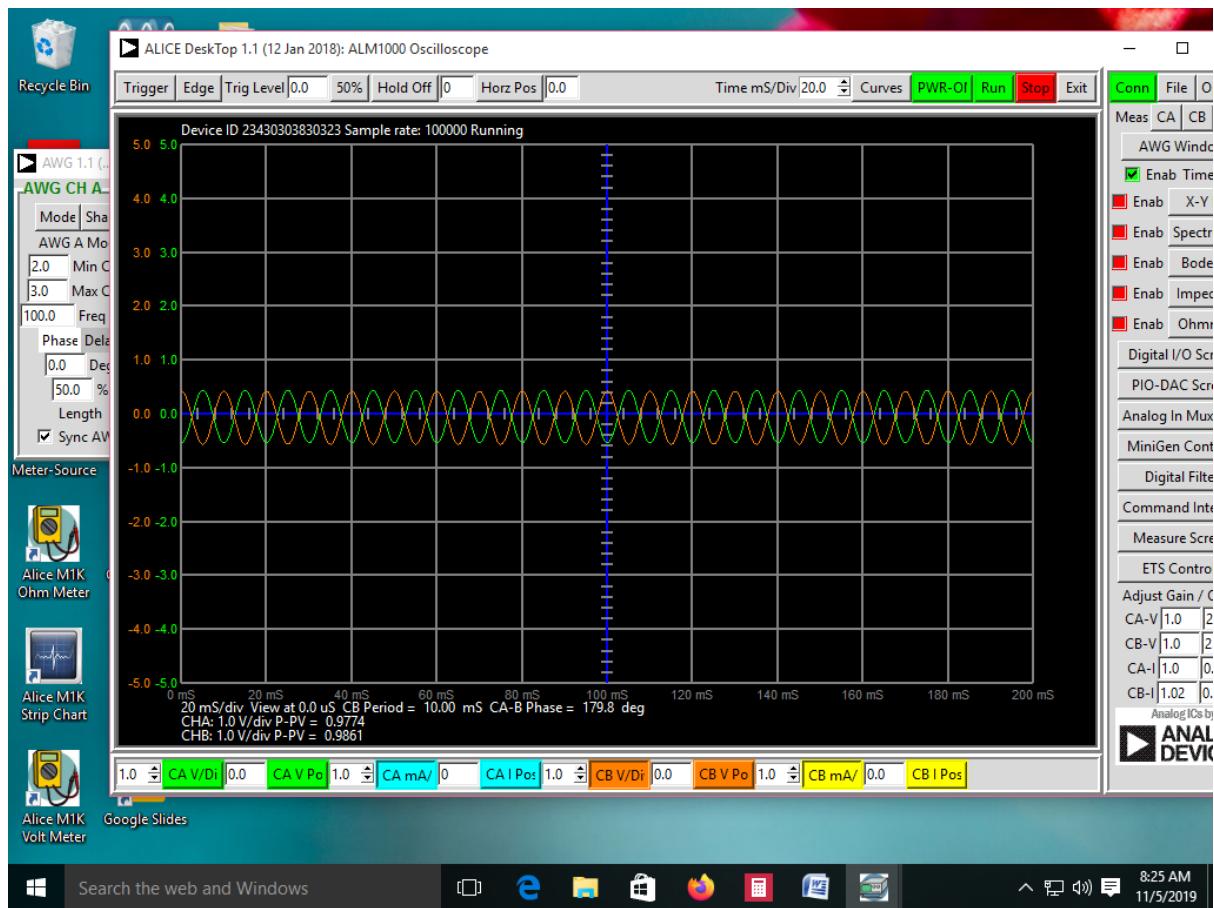

The given wave form is of an inverting op-amp since the waves have a phase difference of 180 degrees. Since the both the amplitudes of the sine waves are equal and the ratio of Channel A : Channel B is almost 1, the gain is 1.

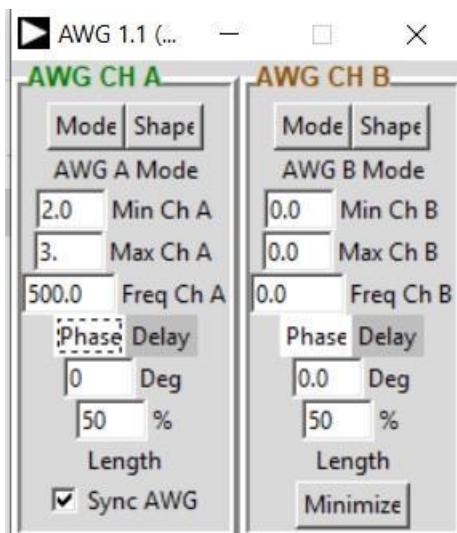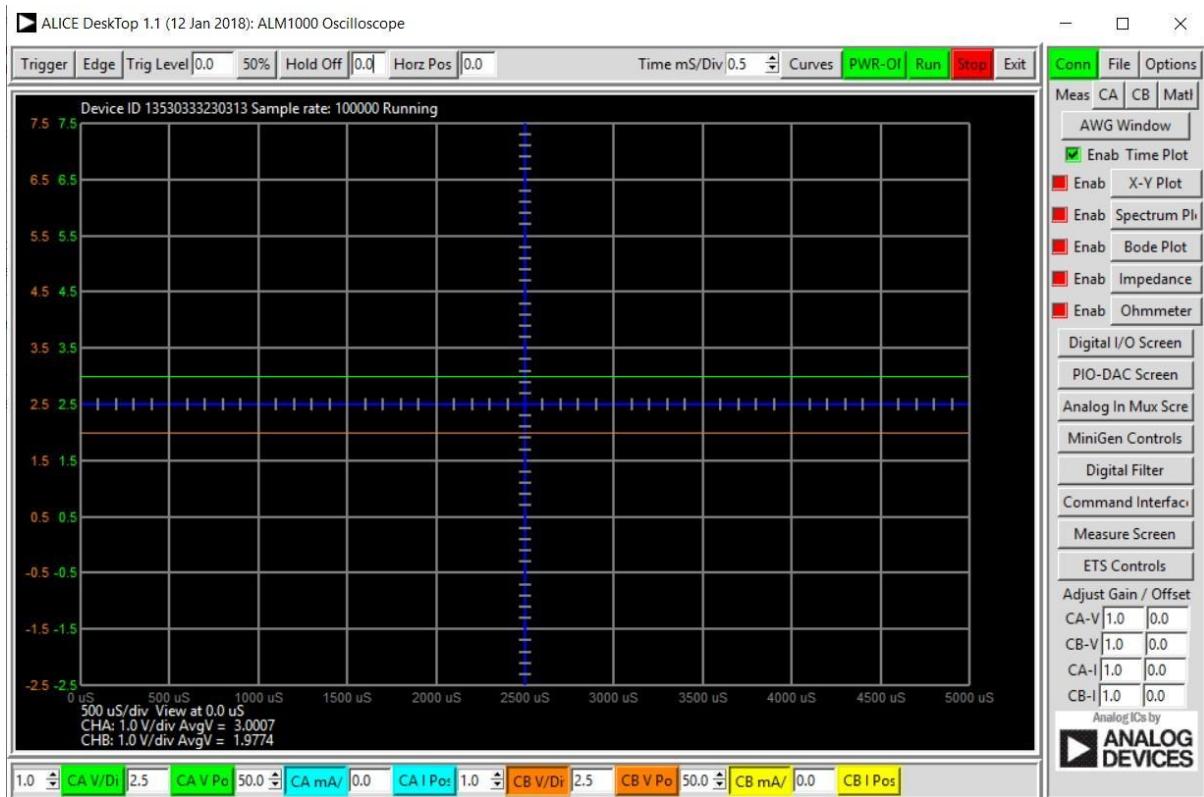When CA-V is changed to 2.0V and 3.0V, waves similar to the ones above are observed but the graphs have been shifted up by 2.5V. When the shape is changed to DC, the sine waves change to a constant straight line parallel to the x-axis.



Reference:

<https://www.danotes.com/electronics/devices-circuits/inverting-and-non-inverting-amplifiers>
<https://electronicsforu.com/resources/learn-electronics/inverting-non-inverting-amplifier-basics>
<https://circuitdigest.com/tutorial/non-inverting-operational-amplifier>
<https://circuitdigest.com/tutorial/inverting-operational-amplifier-op-amp>

Acknowledgment:

We would like to thank Dr. Sowmya V. and Mr Vinod for their contribution to this project.